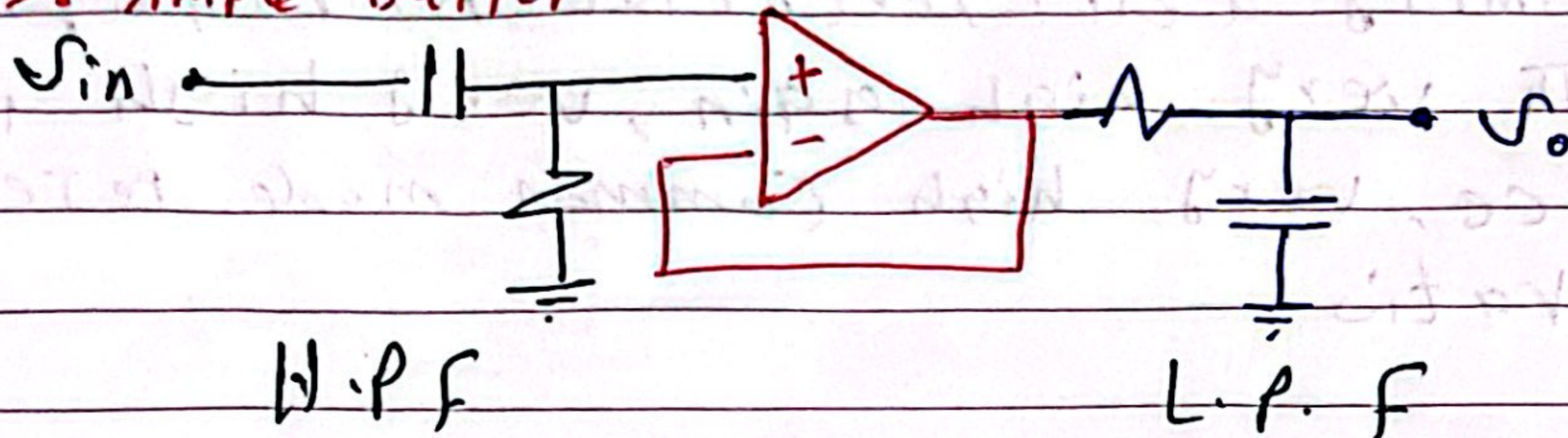


Band Pass filter

"2-Pole Filter"

⇒ Sol 1: Simple Buffer




⇒ Sol 2: Simple LRC

$$\omega_c = \sqrt{\frac{1}{LC}}$$

$$\omega_c = 2\pi f_c$$

$$Q = \frac{1}{R} \sqrt{\frac{L}{C}}$$

$$\rightarrow Q = \frac{f_c}{\Delta f}$$

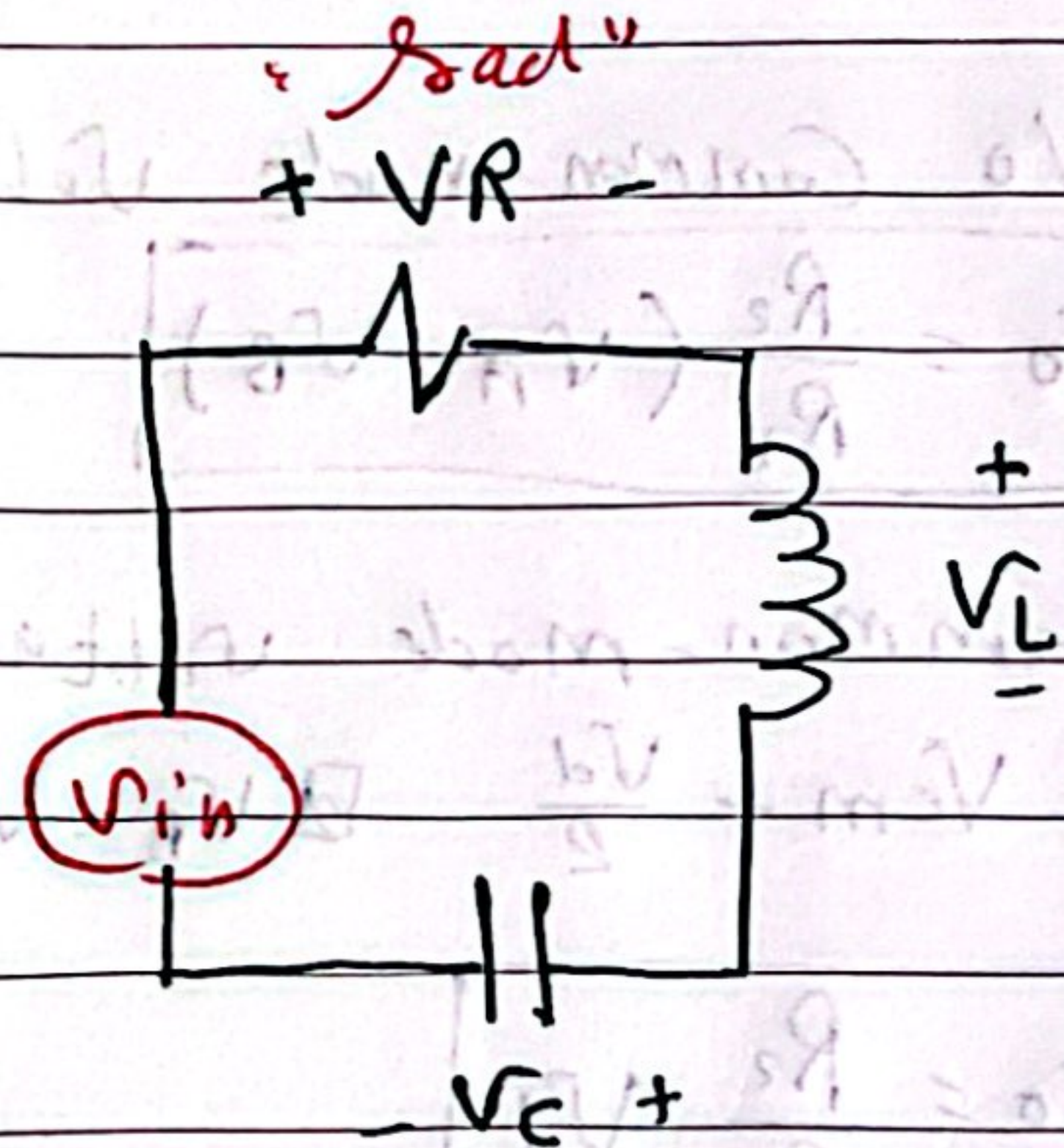

[EX:] Design 2-Pole bandpass filter with bandwidth of 0.1 Hz and $f_c = 1 \text{ Hz}$
load is 100Ω

$$\therefore f_c = \frac{1}{2\pi\sqrt{LC}}$$

$$\therefore Q = \frac{f_c}{\Delta f} = \frac{1}{0.1} = 10$$

$$\therefore 1 = \frac{1}{2\pi\sqrt{LC}} \rightarrow \text{①}$$

$$\therefore 10 = \frac{1}{100} \sqrt{\frac{L}{C}} \rightarrow \text{②}$$

⇒ from ① and ②:

$$L = 159 \text{ H}$$

$$C = 159 \text{ MF}$$