


Instrumental Amp

it is simply a differential Amplifier but with very high gain, very high Impedance, very high Common mode rejection ratio

⇒ Differential Amplifier

Common-Mode Voltage: V_B

$$V_O = \frac{R_2}{R_1} (V_A - V_B)$$

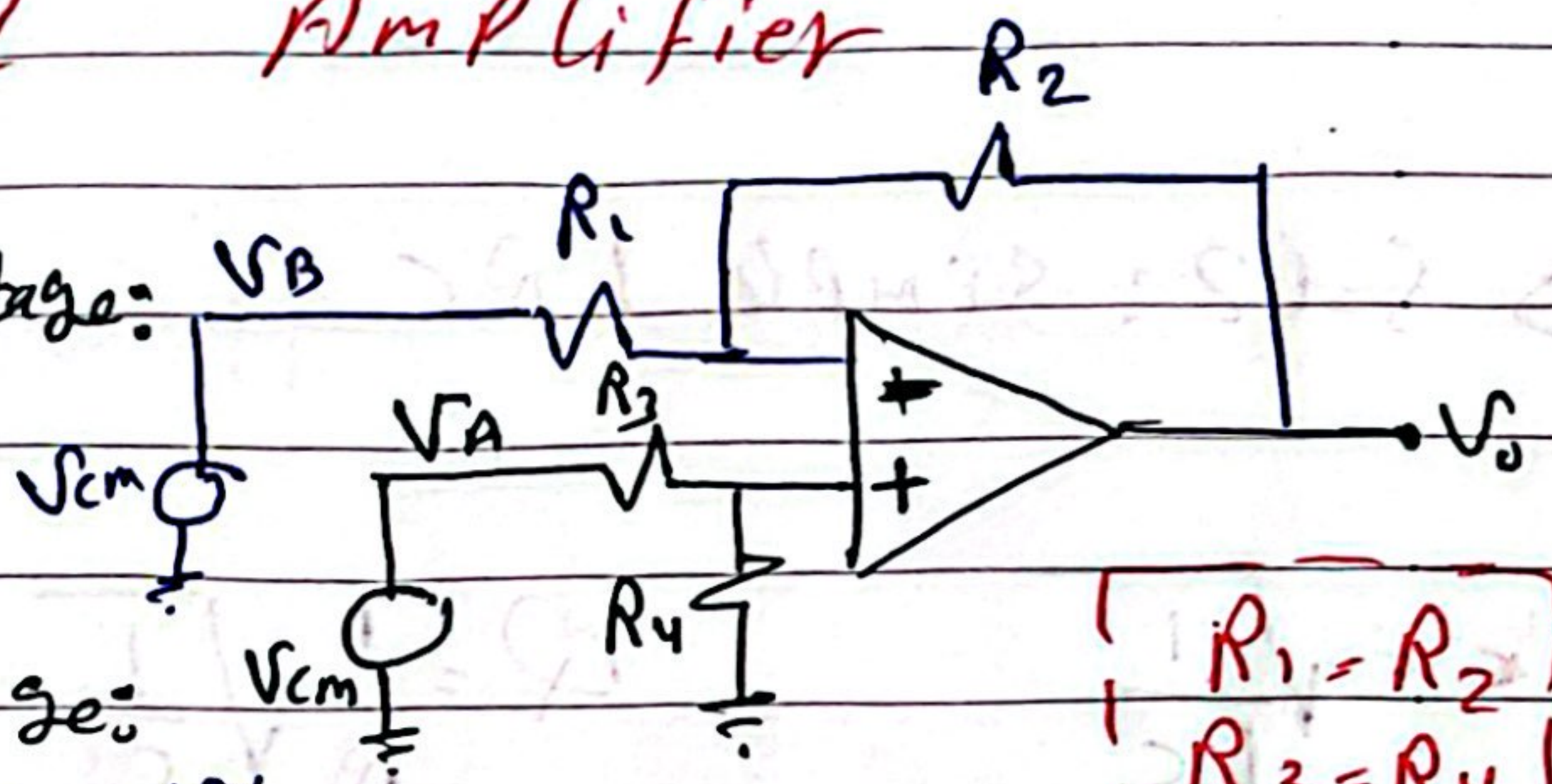


Common-mode voltage: V_{CM}

$$V_A = V_{CM} + \frac{V_d}{2} \quad V_B = V_{CM} - \frac{V_d}{2}$$

$$\begin{cases} R_1 = R_2 \\ R_3 = R_4 \end{cases}$$

$$V_O = \frac{R_2}{R_1} V_d$$

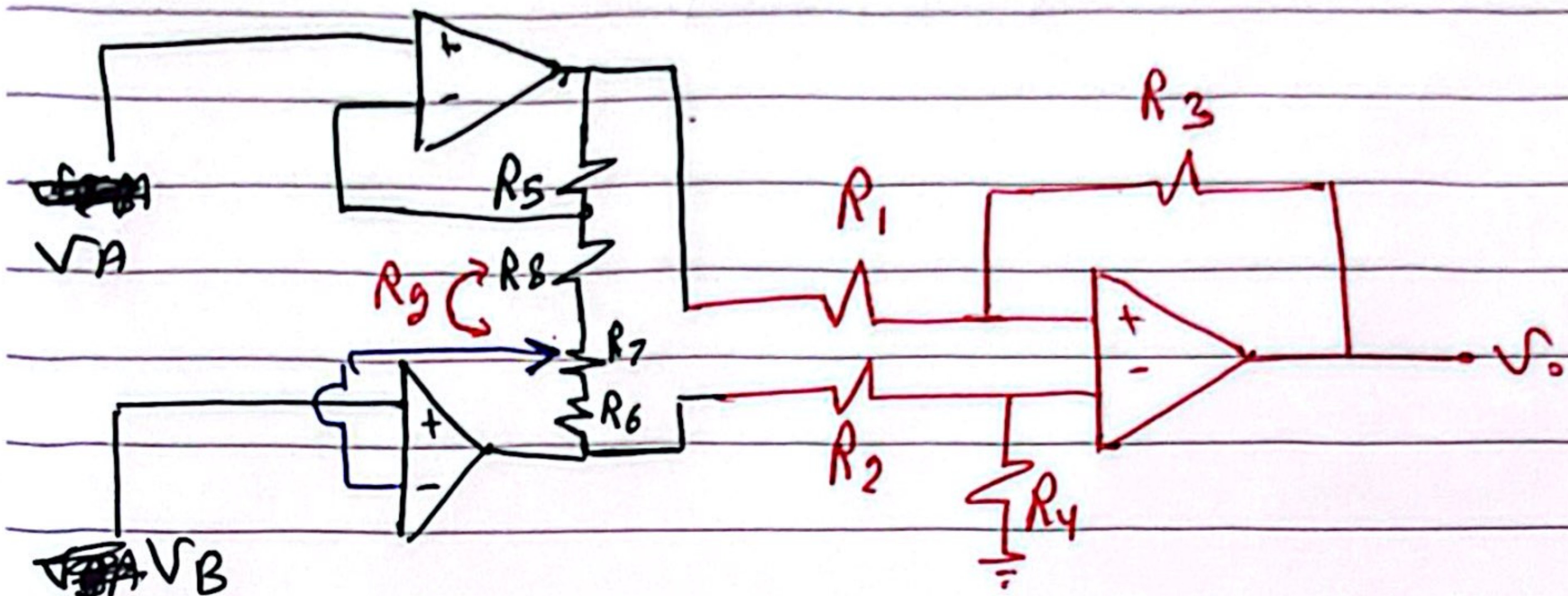we can solve the problem resulted from the mismatch between the resistors pairs by using 2 Buffer Circuits to the inputs But then, you can't change the gain of the diff Amp
Thus, we can use the # Non-Inverting op Amps



$$V_o = \left(1 + \frac{2R_5}{R_g} \right) \left(\frac{R_3}{R_1} \right) (V_A - V_B)$$

⇒ for common mode voltage:

$$V_o = \frac{R_3}{R_1} V_d \quad \#$$

⇒ when: $R_5 = 51k\Omega$, $R_3 = R_1 = 10k\Omega$: —

at $V_A = V_B = 15mV$

at $V_A = 15mV$, $V_B = 10mV$

$$V_o = \frac{R_3}{R_1} V_d = -68 \mu V$$

$$V_o = 9.993 \mu$$

#